


# Report for computer assignment #4

Babak Hosseini Mohtasham

810101408

1.

SR-latch with active low inputs

 

```


1  `timescale 1ns/1ns
2  module q1_sr_latch_1 #(parameter q_inputs_cnt = 2, qb_inputs_cnt=2) (input S, R, S1,R1, output Q, Qb);
3      nand #(q_inputs_cnt*4) n0(Q,S,S1,Qb);
4      nand #(qb_inputs_cnt*4) n1(Qb,R,R1,Q);
5  endmodule

```

```

1  `timescale 1ns/1ns
2  module q1_tb_1();
3      reg s=1'd0;
4      reg r=1'd0;
5      reg clk=1'd1;
6      wire q,qb;
7      q1_sr_latch_1 #(2,2) a1(s,r,clk,clk,q0,qb0);
8      initial begin
9          s=0; r=0;
10         #50; s=0; r=0;
11         #50; s=0; r=0;
12         #50; s=0; r=1;
13         #50; s=0; r=1;
14         #50; s=1; r=0;
15         #50; s=1; r=0;
16         #50; s=0; r=0;
17         #50; s=0; r=0;
18         #50; s=1; r=1;
19         #50; s=1; r=1;
20         #50; s=0; r=0;
21         #50; s=0; r=0;
22         #50;
23     end
24 endmodule


```

 

 2.

```
1 `timescale 1ns/1ns
2 module q2_edge_trigger(input D, clk, output Q, Qb);
3     wire q0,qb0,q1,qb1;
4     wire z=1'd1;
5     q1_sr_latch_1 #(3,2) a0(qb1,D,clk,z,q0,qb0);
6     q1_sr_latch_1 #(2,2) a1(qb0,clk,z,z,q1,qb1);
7     q1_sr_latch_1 #(2,2) a2(qb1,q0,z,z,Q,Qb);
8 endmodule
```

```
1 `timescale 1ns/1ns
2 module q2_tb_1();
3     reg d=1'd0;
4     reg clk=1'd0;
5     wire q,qb;
6     q2_edge_trigger a1(d,clk,q,qb);
7     always #37 clk=~clk;
8     initial begin
9         d=0;
10        #37; d=1;
11        #37; d=1;
12        #28; d=0;
13        #83; d=1;
14        #20;
15        #37; d=0;
16        #22; d=1;
17        #72; d=0;
18        #100; $stop;
19    end
20 endmodule
```



Setup time of 0 to 1=0ns

Setup time of 1 to 0=10ns


Hold time of 0 to 1=0ns

Hold time of 1 to 0=4ns

 3.

```
1 `timescale 1ns/1ns
2 module q3(input D, clk,pre,clr, output Q, Qb);
3     wire q0,qb0,q1,qb1;
4     q1_sr_latch_1 #(3,3) a0(qb1,D,clk,clr,q0,qb0);
5     q1_sr_latch_1 #(3,3) a1(qb0,clk,pre,clr,q1,qb1);
6     q1_sr_latch_1 #(3,3) a2(qb1,q0,pre,clr,Q,Qb);
7 endmodule
```

```
1 `timescale 1ns/1ns
2 module q3_tb_1();
3     reg d=1'd0;
4     reg pre=1'd0;
5     reg clr=1'd0;
6     reg clk=1'd0;
7     wire q,qb;
8     q3 a1(d,clk,~pre,~clr,q,qb);
9     always #37 clk=~clk;
10    initial begin
11        d=0; clr=0; pre=0;
12        #50;
13        #30; d=1;
14        #80; clr=1;
15        #29; d=0; clr=0;
16        #45; pre=1;
17        #20; pre=0;
18        #80; d=1;
19        #80; clr=1; pre=1;
20        #80; pre=0; clr=0;
21        #80; d=0;
22        #100; $stop;
23    end
24 endmodule
```



When D changes from 0 to 1 delay of:

$Q=24$  and  $Q_{\text{bar}}=36\text{ns}$

When D changes from 1 to 0 delay of:

$Q=36$  and  $Q_{\text{bar}}=24\text{ns}$

When CLR changes from 0 to 1 delay of:

$Q=24$  and  $Q_{\text{bar}}=12\text{ns}$

When PRE changes from 0 to 1 delay of:

$Q=12$  and  $Q_{\text{bar}}=24\text{ns}$

When both CLR and PRE change from 0 to 1 the  
delay is:  $12\text{ns}$